



## **Using the Optional Resistor Bank to Improve the Antenna Bandwidth**

**John Pinks**  
Chief Engineer Emeritus  
December 2005

**Nautel Limited**  
10089 Peggy's Cove Road,  
Hackett's Cove, NS, Canada B3Z 3J4  
T.+1.902.823.2233 F.+1.902.823.3183  
info@nautel.com


U.S. customers please contact:

**Nautel Maine, Inc.**  
201 Target Industrial Circle, Bangor ME 04401  
T.+1.207.947.8200 F.+1.207.947.3693  
info@nautel.com


e-mail: support@nautel.com  
**www.nautel.com**
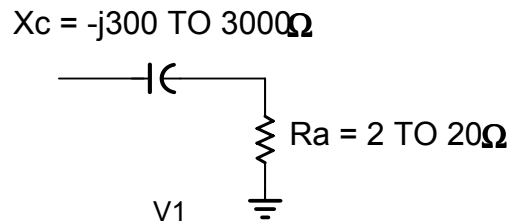
# Using the Optional Resistor Bank to Improve the Antenna Bandwidth

The height of a typical NDB antenna is much shorter than the ideal value. As a result, the antenna input impedance appears as a small resistance in series with a high capacitive reactance.



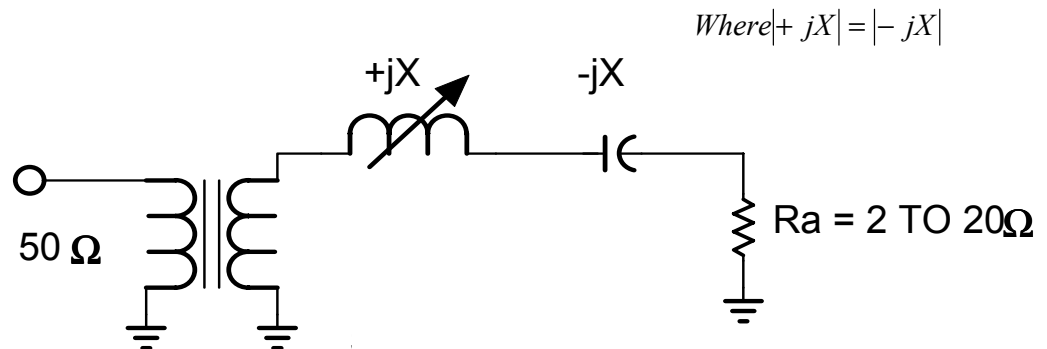The Antenna Tuning Unit resonates the capacitor with a loading coil at the operating carrier frequency ( $F_c$ ) and transforms the resulting low resistance to  $50\Omega$  using an RF transformer.



As a result, the antenna acts as a bandpass filter, tuned to  $F_c$  with a

$$Q \text{ value} = \left( \frac{X}{R} \right)$$

that can vary between  $\left( \frac{3000}{2} \right)$  or 1500 and  $\left( \frac{300}{20} \right)$  or 15.

The resulting antenna bandwidth is given by the expression  $BW = \left( \frac{f_c}{Q} \right)$


Hence, in the worst case condition where  $F_c = 190\text{kHz}$ , and  $Q = 1500$ , the bandwidth would be  $\left( \frac{190}{1500} \right) = 127 \text{ Hz}$ .

Fortunately, with practical antennas, these worst case conditions almost never occur, however,  $Q$  values as high as several hundred and bandwidths less than 1000 Hz are common.

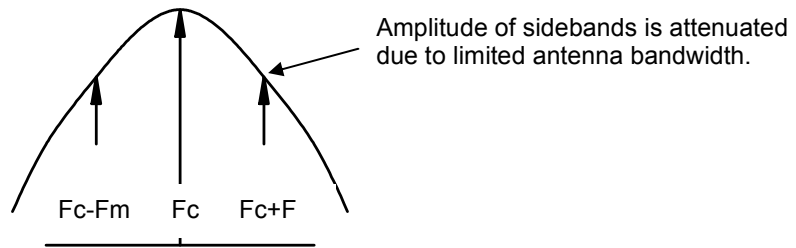
### Necessary Bandwidth

The spectrum of an NDB signal extends to twice the highest modulating frequency and hence is dependent upon the frequency of the identification tones and, where used, the modulating voice signal. 400 Hz identification tones are sometimes used instead of 1020 Hz to minimize the necessary bandwidth.






Result

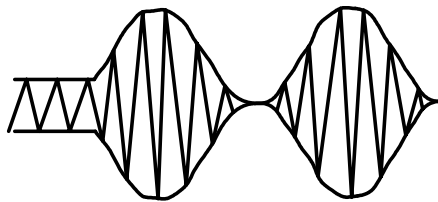


Input to Antenna

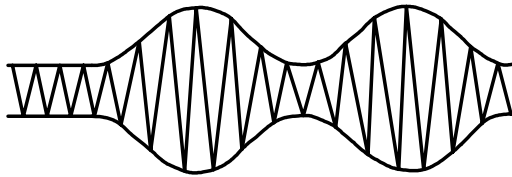

Radiated Signal

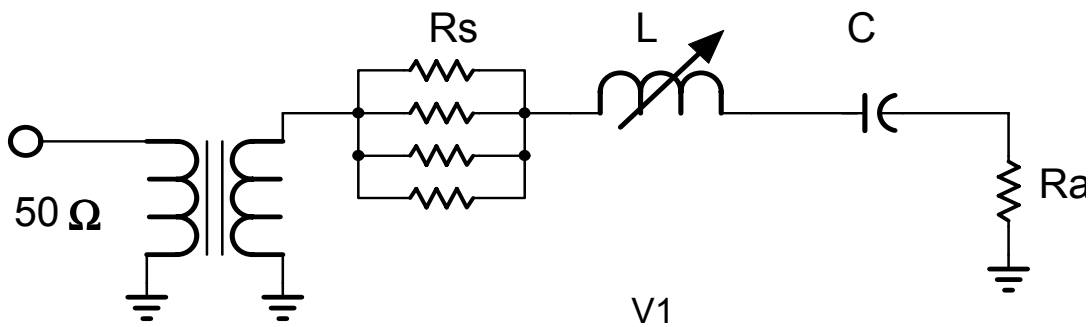As an option, the ATU can contain a built-in resistor group which may be connected in series with the loading coil to lower the Q of the antenna and hence broaden the bandwidth.



To calculate the antenna bandwidth for a particular installation:

1. Determine the loading coil inductance and antenna resistance ( $R_A$ ) from installation records. If the antenna resistance ( $R_A$ ) cannot be obtained from installation records, the following method may be used to determine the antenna resistance ( $R_A$ ):

Note the forward power and antenna current on ATU meter in CW mode (no modulation).

$$\text{Note that Forward Power} = I_a^2 \times R_A$$

$$\text{Calculate } R_A = \frac{\text{Forward Power}}{I_a^2}$$

$$2. \text{ Calculate } X_L = \left( \frac{6.28 \times f_c (\text{kHz}) \times \text{Coil Inductance} (\mu\text{H})}{1000} \right)$$

$$3. \text{ Calculate Antenna } Q_A = \left( \frac{X_L}{R_A} \right)$$

$$4. \text{ Calculate Antenna Bandwidth} = \left( \frac{f_c}{Q_A} \right)$$

Repeat 3 and 4 using  $Q_A = \left( \frac{X_L}{R_A + R_S} \right)$  to determine improved bandwidth.

Note: Use of  $R_S$  will lower the overall antenna efficiency by a factor approximately equal to  $\left( \frac{R_A}{R_A + R_S} \right)$

